

Name: ADITYA BADAYALYA

Enrolment Number: 510819056

COMPUTER ORGANIZATION AND ARCHITECHTURE
LAB(Hy)

ASSIGNMENT-5

1.Design and simulate 4:1 MUX using If-else construct. Use protection for high impedance (Z) states in inputs.

TESTBENCH

```
-- Code your testbench here
library IEEE;
use IEEE.std_logic_1164.all;
entity MUXif is
-- empty
end MUXif;
architecture tb of MUXif is
-- DUT component
component muxi is
port(
    s0: in std_logic;
    s1: in std_logic;
    i0: in std_logic;
    i1: in std_logic;
    i2: in std_logic;
    i3: in std_logic;
    z: out std_logic );
end component;
signal s0,s1,i0,i1,i2,i3,z : std_logic;
```

```
begin
  -- Connect DUT
  DUT: muxi port map(s0,s1,i0,i1,i2,i3,z);
  process
  begin
    i0<='1';
    i1<='0';
    i2<='1';
    i3<='0';

    s0 <= '0';
    s1 <= '0';
    wait for 1 ns;
    s0 <= '0';
    s1 <= '1';
    wait for 1 ns;

    s0 <= '1';
    s1 <= '0';
    wait for 1 ns;

    s0 <= '1';
    s1 <= '1';
    wait for 1 ns;
  end process;
end tb;
```

DESIGN


```
-- Code your design here

library IEEE;
use IEEE.std_logic_1164.all;
entity muxi is port(s0,s1: in
std_logic; i0,i1,i2,i3: in
std_logic;
z: out std_logic);
end muxi;
architecture behavioral of muxi is

begin process(s0,s1,i0,i1,i2,i3)

    begin
    if (s0 = '0' and s1 = '0') then
    z<=i0;
    elsif ( s0 = '0' and s1 = '1') then
    z<=i1;
    elsif ( s0 = '1' and s1 = '0') then
    z<=i2;
    elsif (s0 = '1' and s1 = '1') then
    z<=i3;
    end if;
    end process;

end behavioral;
```

 

2. Design and simulate 4:1 MUX using Case construct. Use protection for high impedance (Z) states in inputs.

TESTBENCH

```
-- Code your testbench here
library IEEE;
use IEEE.std_logic_1164.all;
entity MUXcase is
-- empty
end MUXcase;
architecture tb of MUXcase is
-- DUT component
component muxcas is
port(
    s0: in std_logic;
    s1: in std_logic;
    i0: in std_logic;
    i1: in std_logic;
    i2: in std_logic;
    i3: in std_logic;
    z: out std_logic );
end component;
signal s0,s1,i0,i1,i2,i3,z : std_logic;
begin
-- Connect DUT
```

```
DUT: muxcas port map(s0,s1,i0,i1,i2,i3,z);
```

```
process
```

```
begin
```

```
i0<='1';
```

```
i1<='0';
```

```
i2<='1';
```

```
i3<='0';
```

```
s0 <= '0';
```

```
s1 <= '0';
```

```
wait for 1 ns;
```

```
s0 <= '0';
```

```
s1 <= '1';
```

```
wait for 1 ns;
```

```
s0 <= '1';
```

```
s1 <= '0';
```

```
wait for 1 ns;
```

```
s0 <= '1';
```

```
s1 <= '1';
```

```
wait for 1 ns;
```

```
end process;
```

```
end tb;
```

DESIGN

-- Code your design here

library IEEE;

use IEEE.std_logic_1164.all; use

ieee.numeric_std.all; entity muxcas is

port(s0,s1,i0,i1,i2,i3: in std_logic; z:

out std_logic);

end muxcas;

architecture behavioral of muxcas is

 signal v_CONCATENATE : std_logic_vector(1 downto 0);

begin

 v_CONCATENATE <=s0 & s1;

 process (v_CONCATENATE,s0,s1)

 begin

 case (v_CONCATENATE) is

 when ("00") =>

 z<=i0;

 when ("01") =>

 z<=i1;

 when ("10") =>

 z<=i2;

 when ("11") =>


 z<=i3;

 when others =>

 z<='0';

 end case;


```
end process;  
end behavioral;
```

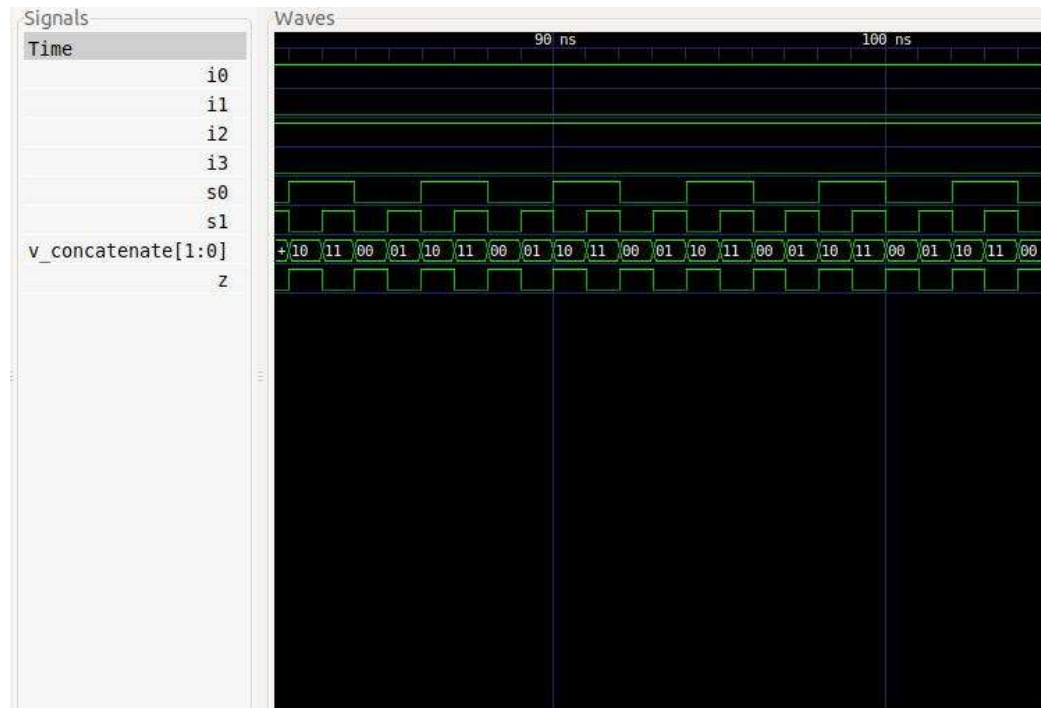

3.Design and simulate 3-to-8 DECODER using If-else construct.

TESTBENCH

```
-- Code your testbench here
library IEEE;
use IEEE.std_logic_1164.all;
entity decoder38 is
-- empty
end decoder38;
architecture tb of decoder38 is
-- DUT component
component dec3 is
port(
input: in std_logic_vector(2 downto 0):=(others=>'0');
output: out std_logic_vector(7 downto 0):=(others=>'0') );

end component;
signal input: std_logic_vector(2 downto 0);
signal output: std_logic_vector(7 downto 0);
begin
-- Connect DUT
DUT: dec3 port map(input,output);
process
begin
input<="000"; --input = 0.
```

```

wait for 2 ns;
input<="001"; --input = 1.
wait for 2 ns;
input<="010"; --input = 2.
wait for 2 ns;
input<="011"; --input = 3.
wait for 2 ns;
input<="100"; --input = 4.
wait for 2 ns;
input<="101"; --input = 5.
wait for 2 ns;
input<="110"; --input = 6.
wait for 2 ns;
input<="111"; --input = 7.
    end process;
end tb;

```

DESIGN

```

--libraries to be used are specified here
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--entity declaration with port definitions entity
dec3 is
port( input : in std_logic_vector(2 downto 0); --3 bit input output :
      out std_logic_vector(7 downto 0) -- 8 bit output );

```

```
end dec3;
--architecture of entity
architecture Behavioral of dec3 is
begin
    process(input)
    begin
        if input = "000" then
            output <= "00000001";
        elsif input = "001" then
            output<="00000010";
        elsif input = "010" then
            output<="00000100";
        elsif input = "011" then
            output<="00001000";
        elsif input = "100" then
            output<="00010000";
        elsif input = "101" then
            output<="00100000";
        elsif input = "110" then
            output<="01000000";
        elsif input = "111" then
            output<="10000000";
        end if;
    end process;
end Behavioral;
```

Signals

Time

input[2:0]

output[7:0]



4. Design and simulate 3-to-8 DECODER using Case construct. Use protection for high impedance (Z) states in inputs.

TESTBENCH

```
-- Code your testbench here
library IEEE;
use IEEE.std_logic_1164.all;
entity deccase is
-- empty
end deccase ;
architecture tb of deccase is
-- DUT component
component DECc is
port(
input: in std_logic_vector(2 downto 0):=(others=>'0');
output: out std_logic_vector(7 downto 0):=(others=>'0') );

end component;
signal input: std_logic_vector(2 downto 0);
signal output: std_logic_vector(7 downto 0);
begin
-- Connect DUT
DUT: DECc port map(input,output);
process
begin
```

```

input<="000"; --input = 0.
wait for 2 ns;
input<="001"; --input = 1.
wait for 2 ns;
input<="010"; --input = 2.
wait for 2 ns;
input<="011"; --input = 3.
wait for 2 ns;
input<="100"; --input = 4.
wait for 2 ns;
input<="101"; --input = 5.
wait for 2 ns;
input<="110"; --input = 6.
wait for 2 ns;
input<="111"; --input = 7.
    end process;
end tb;

```

DESIGN

```

--libraries to be used are specified here
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--entity declaration with port definitions entity
DECc is
port( input : in std_logic_vector(2 downto 0); --3 bit input output :
      out std_logic_vector(7 downto 0) -- 8 bit output );

```

```
end DECc ;  
--architecture of entity  
architecture Behavioral of DECc is  
begin  
  process(input)  
  begin  
    case (input) is  
      when "000"=>  
        output<="00000001";  
      when "001"=>  
        output<="00000010";  
      when "010"=>  
        output<="00000100";  
      when "011"=>  
        output<="00001000";  
      when "100"=>  
        output<="00010000";  
      when "101"=>  
        output<="00100000";  
      when "110"=>  
        output<="01000000";  
      when "111"=>  
        output<="10000000";  
      when others=>  
        output<="00000000";  
    end case;  
  end process;  
end Behavioral;
```



```
Time
input[2:0]
output[7:0]
```

30 ns					40 ns					50 ns					60 ns					70 ns					
110	000	001	010	011	100	101	110	000	001	010	011	100	101	110	000	001	010	011	100	101	110	000	001	010	011
40	01	02	04	08	10	20	40	01	02	04	08	10	20	40	01	02	04	08	10	20	40	01	02	04	08